



→ Basics of electrical engineering

Unit → 1

~~~~~

### - Resistance

Opposition offered by a material to flow of electric current

$$R = \rho \frac{L}{A}$$

By ohm's law,  $R = \frac{V}{I}$

### → Ohm's Law

Acc to ohm's law, potential diff across any 2 points of a conductor will be directly proportional to the current flowing through it when physical conditions

$$V \propto I$$


like temp

$$V = IR$$

### → Kirchhoff's Laws

- KVL (Based on conservation of energy) In any closed ckt (mesh) the algebraic sum of emf & voltage drops is zero.


$$\sum \text{Emf} + \sum IR = 0$$

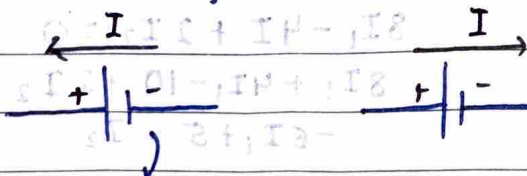

→ drop in potential (-ve)

Rise in potential

(+ve)

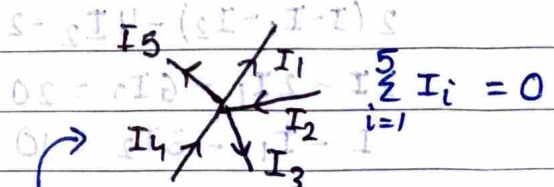


- KCL (Conservation of charges)

The algebraic sum of all currents meeting at a pt or junction will be zero

$$\sum I = 0$$




## → Mesh Analysis method

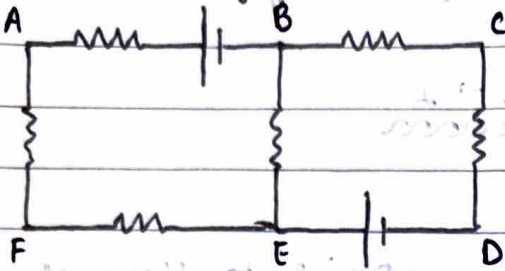

Mesh is a closed path on electrical circuit via which current can flow but there is no other closed path in it like ABEF & BCDE → Mesh  
But loop can contain closed path within it too like ABEF, BCDE & ACDF → Loop

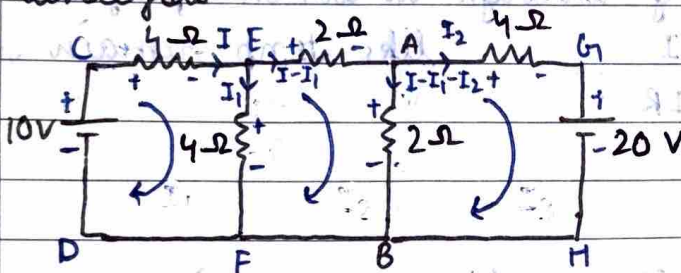Q. Calculate current in AB of 2-Ω using mesh analysis



In mesh CEDF, 2m FEAB

Applying KVL

$$10 - 4I_1 - 4I_1 = 0$$

$$4I_1 + 4I_1 = 10$$

$$4I_1 = 10 - 4I_1$$

In AGHBV

$$2(I_1 - I_2) - 4I_2 - 20 = 0$$

$$2I_1 - 2I_2 - 6I_2 = 20$$

$$I_1 - I_2 - 3I_2 = 10$$

$$\frac{5 - 2I_2}{2} - I_2 = 15 + 18I_2 = 10$$

$$5 - 2I_2 + 36I_2 + 30 = 20$$

$$-40I_2 = -25$$

$$I_2 = 5/8 \text{ A}$$

$$4I_1 - 2(I_1 - I_2) - 2(I_1 - I_2) = 0$$

$$4I_1 - 2I_1 + 2I_2 - 2I_1 + 2I_2 = 0$$

$$8I_1 - 4I_1 + 2I_2 = 0$$

$$8I_1 + 4I_1 - 10 + 2I_2 = 0$$

$$-6I_1 + 5 = I_2$$

$$4I_1 = 10 - 5/2 = 15/2$$

$$I_1 = 15/8 \text{ A}$$

$$I_2 = -\frac{15}{4} + \frac{20}{4} = \frac{5}{4} \text{ A}$$

$$I_{AB} = \frac{15}{8} - \frac{5}{8} = \frac{10}{8}$$





$$5 + 32 I_1 = 50$$

$$32 I_1 = 45$$


$$I_1 = \frac{45}{32} = 1.40 \text{ A}$$

$$I_2 = -3.4 \text{ A}$$

$$I = 1.2 \text{ A}$$

$$I_{AB} = I - I_1 - I_2 = 1.2 - 1.4 + 3.4 = 3.2 \text{ A}$$

Q

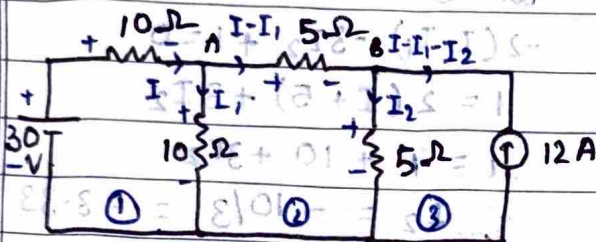

5 Ω resistor

In ①

$$30 - 10I - 10I_1 = 0$$

$$I_1 + I = 3 - \text{①}$$

$$I_1 = 3 - I$$

In ②  $8 \times 10^3 I = 0.2 \text{ V}$ 

$$10I_1 - 5I + 5I_2 - 5I_2 = 0$$

$$15I_1 - 5I - 5I_2 = 0$$

$$45 - 15I - 5I = 5I_2$$

$$9 - 4I = I_2 - \text{②}$$

In ③ since we have a current source so overall current in loop ③ is  $-12 \text{ A}$

$$I - I_1 - I_2 = -12$$

$$I + I - 3 + 4I - 9 = -12$$

$$6I - 12 = -12$$

$$4I = 0 \text{ A}$$


$$\Rightarrow I_2 = 9 \text{ A}$$

$$\Rightarrow I_1 = 3 \text{ A}$$

$$I_{5\Omega} = I - I_1 = -3 \text{ A}$$

? Q

voltage across  $3\Omega$

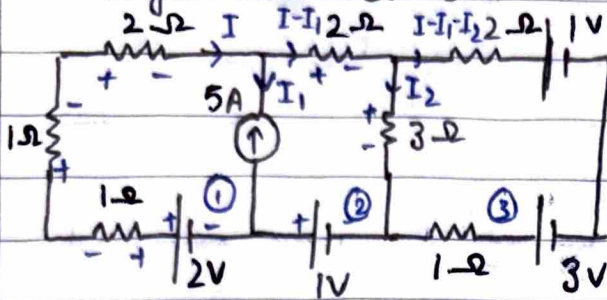

clearly  $I_1 = -5A$  in loop ① in ②

$$-I - 2I + 2 - I = 0$$

$$2 = 4I$$

$$I = 0.5A$$

$$-2(I - I_1) - 3I_2 + 1 = 0$$

$$1 = 2(I + 5) + 3I_2$$

$$1 = 2I + 10 + 3I_2$$


$$I_2 = -10/3 = -3.33$$

$$V_{3\Omega} = I_{3\Omega} \times 3$$

$$V_{3\Omega} = \frac{10}{3} \times 3 = 10V$$

→ Junction & Node

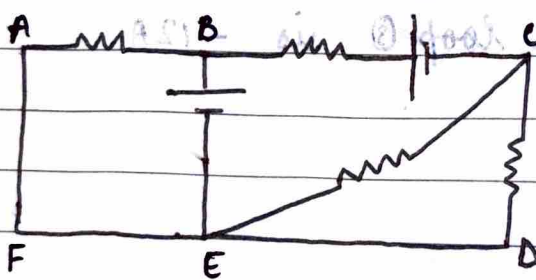Junction is where 3 or more than 3 branches combine but 2 or more than 2 combine at node.



B → node

C → node

D → node

B & C → principle nodes

$$V_{BC} = V_{CD}$$

$$V_{BC} = V_{CD}$$

$$V_{BC} = V_{CD}$$


$$V_{BC} = V_{CD}$$





- steps to solve using nodal analysis
1. identify principle nodes / junctions
  2. assign a junction potential w.r.t assigned reference junction value  $V_0 = 0V$
  3. Assuming all currents in outgoing direction from each junction from KCL eq
  4. solve to calculate junction potentials
  5. Find required quantity

Q Current in  $3\Omega$

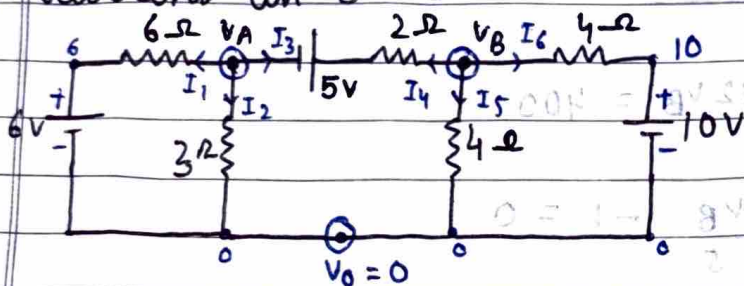

$$I_1 = \frac{V_A - V_0 - 6}{6} \quad \text{Pot. diff} = \frac{V_A - 6}{6} \quad \text{Resistance}$$

KCL at A

$$\frac{V_A - 6}{6} + \frac{V_A + 5 - V_B}{2} + \frac{V_A}{3} = 0$$

$$V_A - 6 + 3V_A + 15 - 3V_B + 2V_A = 0$$

$$6V_A - 3V_B + 9 = 0$$

$$2V_A + 3 = V_B$$

KCL at B

$$\frac{V_B}{4} + \frac{V_B - 10}{4} + \frac{V_B - 5 - V_A}{2} = 0$$

$$2V_B - 10 + 2V_B - 2V_A - 10 = 0$$

$$4V_B - 2V_A = 20$$

$$2V_B - V_A = 10$$

$$4V_A + 6 - V_A = 10$$


$$3V_A = 4$$

$$V_A = 4/3 \quad \Rightarrow V_B = 17/3 V$$

$$I_{6\Omega} = \frac{V_A}{3} = \frac{4}{9} A$$



Q Current in  $4\Omega$  branch

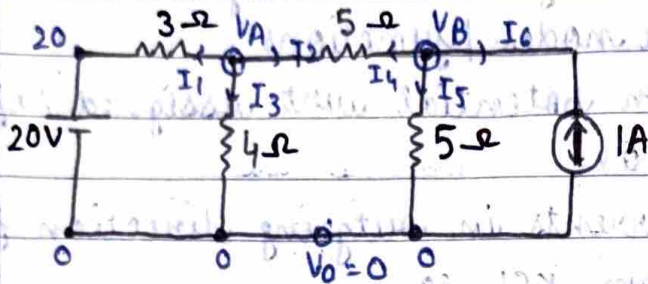

KCL at A  
 $\frac{V_A - 20}{3} + \frac{V_A}{4} + \frac{V_A - V_B}{5} = 0$

$$20V_A - 400 + 15V_A + 12V_A - 12V_B = 0$$

$$47V_A - 12V_B = 400$$

$$\frac{-V_A + V_B}{5} + \frac{V_B}{5} - 1 = 0$$

$$\frac{V_A - 5}{5} = 1$$

$$V_A = 5V$$

$$235 - 12V_B = 400$$

$$V_B = -13.75V$$

$$I_{4\Omega} = \frac{V_A}{4} = \frac{5}{4} = 1.25A$$

$$2V_B - V_A - 5 = 0$$

on solving

$$V_A = 9.02V$$

$$V_B = 2.012V$$

$$I_{4\Omega} = \frac{V_A}{4} = \frac{9.02}{4} = 2.25A$$


$$A \frac{V}{\Omega} = \frac{V}{\Omega}$$




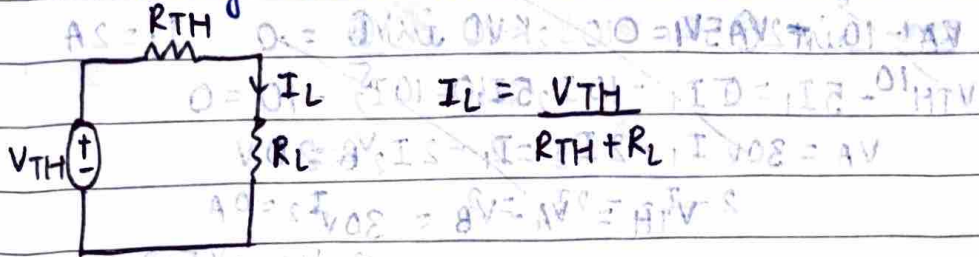
## → Thevenin's Theorem

Any linear bilateral network irrespective of its complexities can be reduced into thevenin equivalent circuit having the Thevenin's open ckt voltage  $V_{TH}$  in series with Thevenin's equivalent resistance  $R_{TH}$  along with load resistance  $R_L$ .




## → Steps to solve

1. Identify load  $R_L$  (Jiska data nikalna k)
2. Remove  $R_L$  & calculate open ckt potential across two open ends. This will be  $V_{TH}$
3. Again remove load resistance & replace all active sources by internal resistances
4. Calculate eq. resistance across open ends, its  $R_{TH}$
5. Draw Thevenin eq. ckt
6. Calculate  $I_L$

3. → voltage → close line  
current → open ckt

## Q Current via 1- $\Omega$ resistor

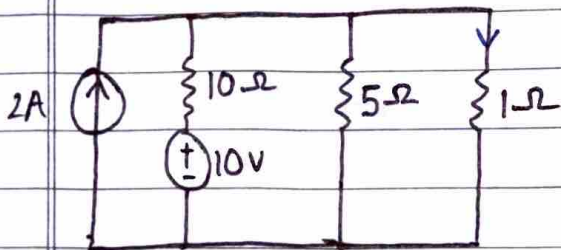


$$R_L = 1\text{-}\Omega$$

$$V_{OC} = 10V$$

$$V_{OC} = 10V = 10V$$


Removing  $R_L$

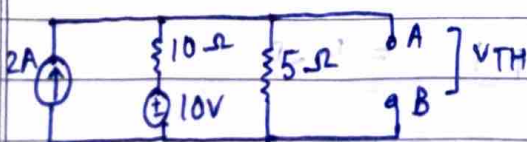

$$I_{TH} = 10V$$

$$I_{TH} = 10V$$

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

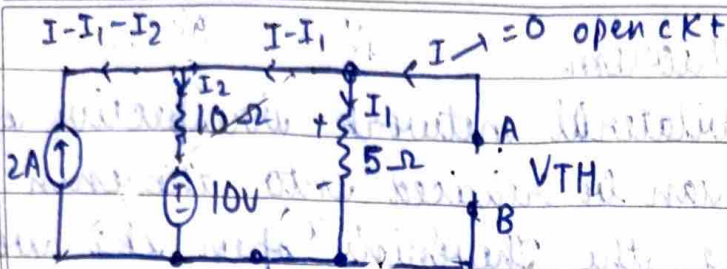

clearly  $I - I_1 - I_2 = -2$   $I = 0 \text{ KCL} \Rightarrow I_1 + I_2 = 2$

$5I_1 - 10I_2 - 10 = 0 \Rightarrow 5I_1 - 10I_2 = 10$   $I_1 = 2A$



$5I_1 - 10I_2 = 10$

$VA = 300 I_1 - 2I_2 = 2 \Rightarrow 300 I_1 - 2I_2 = 2$

$2 - I_2 = 2I_1 \Rightarrow I_2 = 0A$

$\Rightarrow V_{TH} = 5 \times 2 = 10V$

Q I when  $R_L = 6\Omega$  &  $16\Omega$

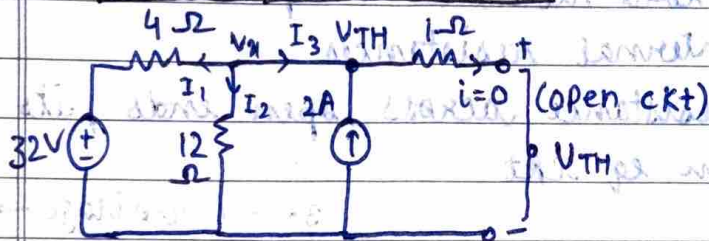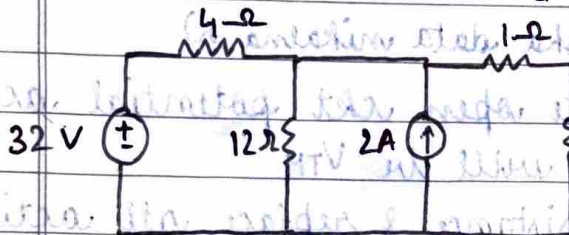


$\frac{Vx - 32}{4} + \frac{Vx}{12} - 2 = 0$

$3Vx - 96 + Vx = 24$

$4x = 120 \Rightarrow$

$Vx = 30V$

$V_{TH} = Vx = 30V$

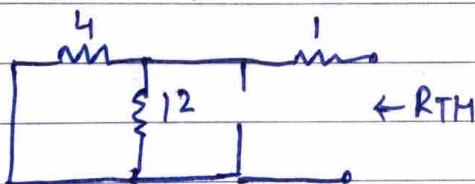

$R_{TH} = \frac{4 \times 12}{4 + 12} + 1 = 4\Omega$


$I_{6\Omega} = \frac{30}{10} = 3A$

$I_{16\Omega} = \frac{30}{20} = 1.5A$




Q

$$I_{50\Omega} = ?$$

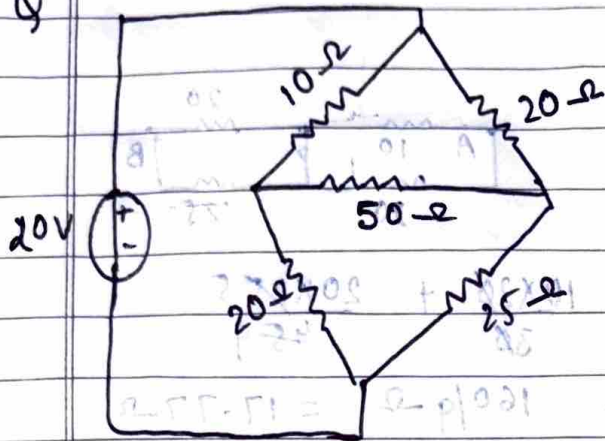

$$R_L = 50\Omega$$

Remove  $R_L$

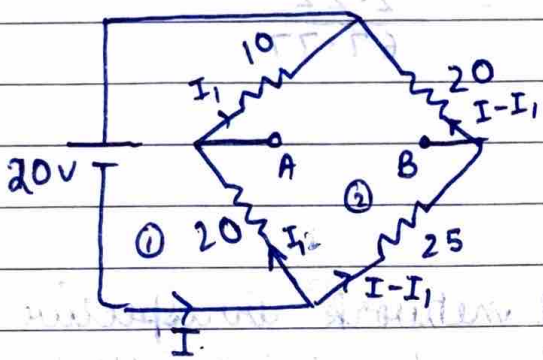

KVL in ①

KVL in ②

$$20 - 10I_1 - 20I_1 = 0$$

$$-20I_1 - 10I_1 + 20(I - I_1) + 25(I - I_1) = 0$$

$$30I_1 = 20$$

$$I_1 = 2/3 \text{ A}$$

$$-50I_1 - 25I_1 + 45I = 0$$


$$I_1 = 0.66 \text{ A}$$

$$945I = \frac{75 \times 2}{255}$$

$$I = 10/9 \text{ A}$$

$$I - I_1 = 0.44$$



$$I = 1.1 \text{ A}$$

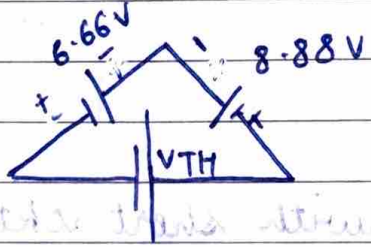

$$I - V_{TH} - 6.66 + 8.88 = 0$$

$$-V_{TH} = -2.22 \text{ V}$$

$$V_{TH} = 2.22 \text{ V}$$

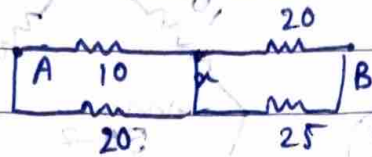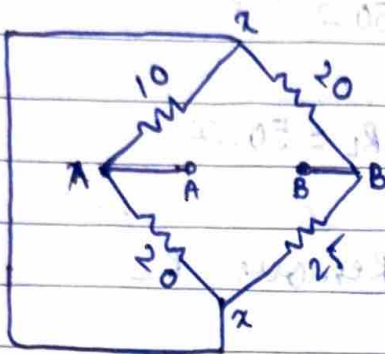

$$\frac{10 \times 20}{30} + \frac{20 \times 25}{45}$$

$$20/3 + 100/9 = 160/9 \Omega = 17.77 \Omega$$

$$\Rightarrow I_L = \frac{2.22}{17.77 + 50} = \frac{2.22}{67.77} = 0.032 \text{ A}$$

### → Norton's Theorem

Any linear bilateral network irrespective of its complexities can be reduced into Norton's equivalent circuit having Norton's short ckt current  $I_N$  in parallel with Norton's equivalent resistance in parallel with  $R_L$ .




$$I_L = \frac{I_N R_N}{R_N + R_L}$$

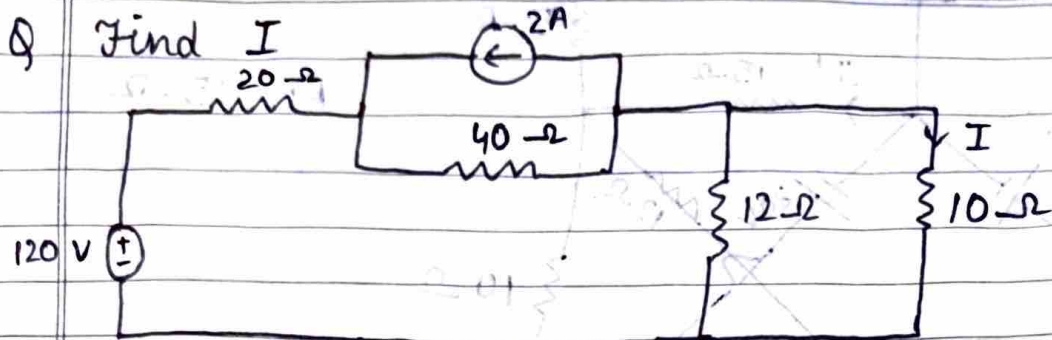
### → Steps

- Find  $R_L$  & replace it with short ckt branch
- Current via this short-ckted branch is  $I_N$
- Remove  $R_L$  & replace the active sources by internal resistance & find  $R_N = V_{OC}/I_N$
- Draw Norton equivalent ckt
- Calculate  $I_L = \frac{I_N R_N}{R_N + R_L}$





$$R_L = 10\Omega$$

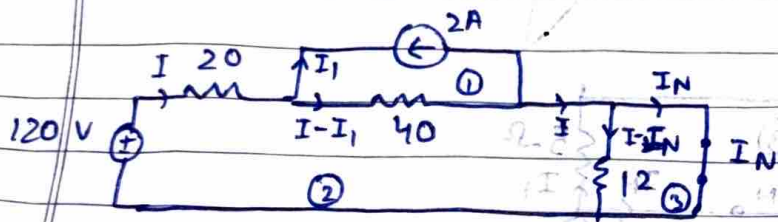

$$I_1 = -2A$$

$$120 - 20I - 40(I - I_1) - 12(I - I_N) = 0$$

$$120 - 20I - 40I + 40I_1 - 12I + 12I_N = 0$$

$$120 - 72I - 80 + 12I_N = 0$$


$$40 = 72I - 12I_N$$

$$10 = 18I - 3I_N \quad \text{--- (1)}$$

$$12(I - I_N) = 0 \quad 0 = 0.6 + 0.5 - (0.1I - 0.1I - 0.1I) \quad 0.1I = 0.1$$


$$I = I_N$$

$$\Rightarrow I = 2/3 A = I_N$$

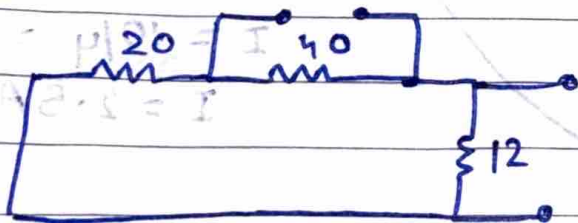


$$I_L = \frac{2/3 \times 10}{10 + 10} = \frac{2/3 \times 10}{20}$$

$$= \frac{1}{3} A = 0.33 A$$

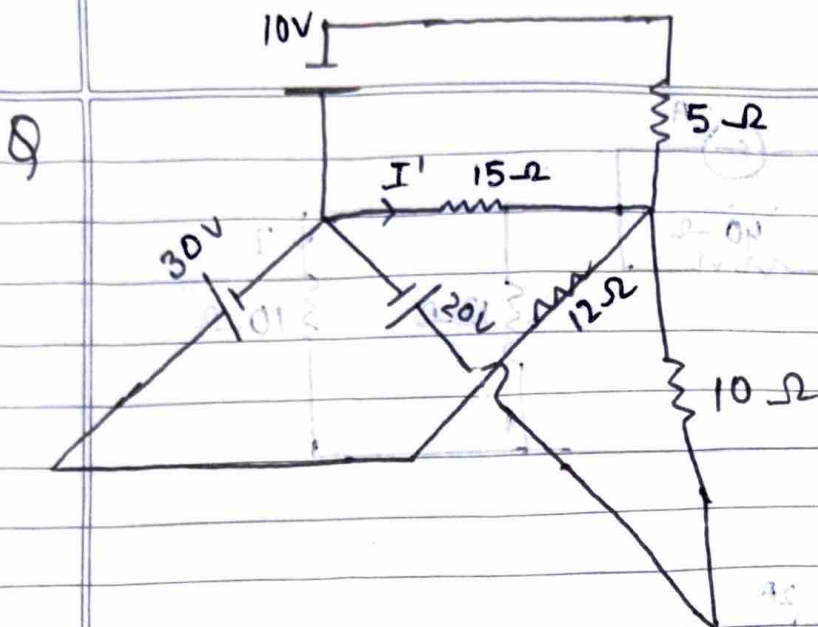

$$R_L = 15\Omega$$

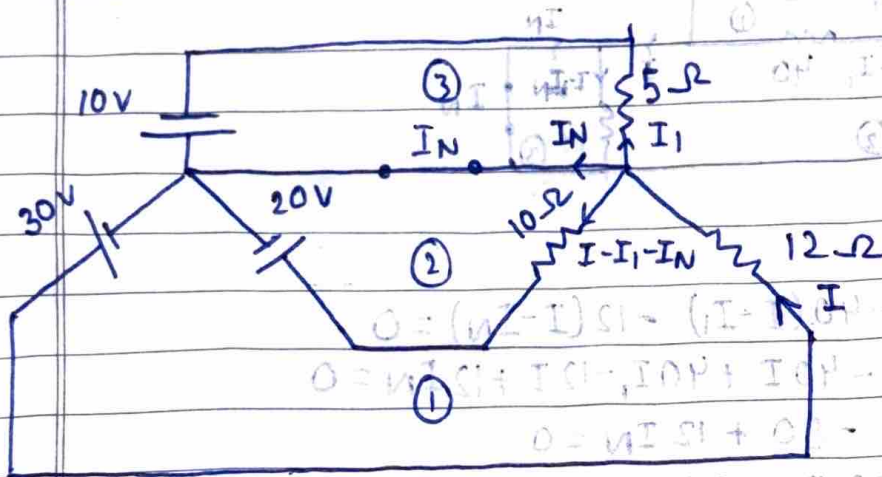

In ①

$$-12I - 10(I - I_1 - I_N) - 20 + 30 = 0$$

$$-22I + 10I_1 + 10I_N + 10 = 0$$

In ②

$$20 + 10(I - I_1 - I_N) = 0$$

$$I_1 + I_N - I = 2$$

$$I_1 + I_N = I + 2$$

$$\Rightarrow I_1 + I_N = 4.5A$$

In ③

$$-10 + 5I_1 = 0$$

$$I_1 = 2A$$

$$① - 12I - 10(I - I_1 - I_N) = 0$$

$$0 = (12I - I_1 - I_N)$$

$$12I = I_1 + I_N$$

$$12I = 30$$


$$I = 30/12 = 2.5A$$

$$I = 2.5A$$

$$I = 2.5A$$

$$\Rightarrow I_N = 2.5A$$



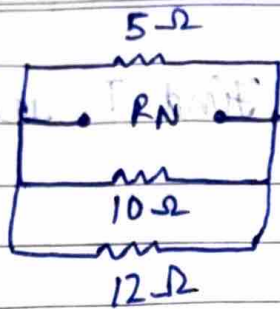

$$5 // 10 \rightarrow 10/3$$

$$10/3 // 12$$

$$\frac{10 \times 12}{8} = \frac{120}{8} = \frac{60}{4} = 15 \Omega$$

$$RN = \frac{10 + 36}{8} = 6 \Omega$$

$$RN = 2.608 \Omega$$



$$I_L = \frac{2.5 \times 2.608}{2.608 + 15} = \frac{2.5 \times 2.608}{17.608} = 0.370 A$$

### → Super Position Theorem

In any linear bilateral multisource network the current / voltage across any branch can be calculated by taking <sup>sum of values</sup> one source at a time & replacing other active sources by internal resistance.
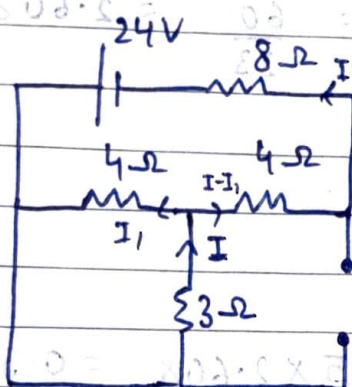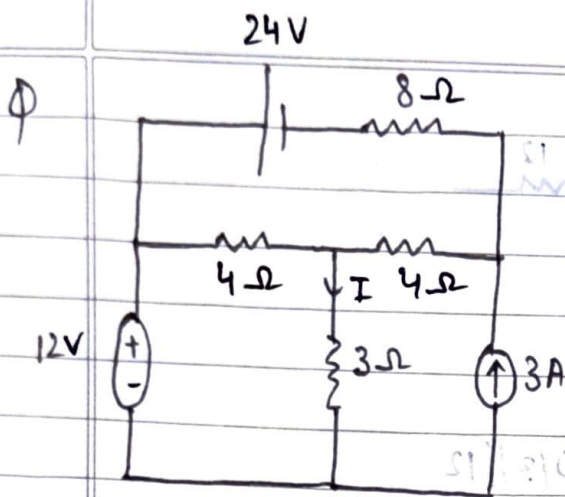
### → Steps


- Find branch, quantity & active source
- Take 1 & replace other by int resistance
- Calculate quantity for that source
- Repeat for all sources
- Sum algebraically



$$-3I - 4I_1 = 0$$

$$3I + 4I_1 = 0$$

$$3I = -4I_1$$

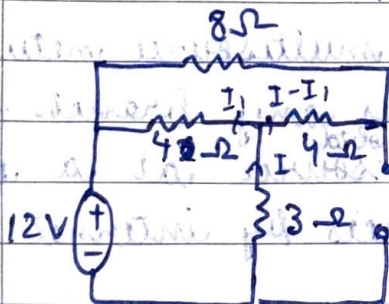

$$-24 + 8(I - I_1) + 4(I - I_1) - 4I_1 = 0$$

$$-24 + 12I - 16I_1 = 0$$

$$6 = 3I - 4I_1$$

$$-8I_1 = 6$$

$$I_1 = -3/4 \text{ A}$$

$$I = 2 \text{ A}$$

$$-4(I - I_1) - 8(I - I_1) + 4I_1 = 0$$

$$3I - 3I_1 = I_1$$

$$4I_1 = 3I$$


$$-3I - 4I_1 - 12 = 0$$

$$3I + 4I_1 + 12 = 0$$

$$8I_1 = -12$$

$$I_1 = -3/2$$

$$I = -2 \text{ A}$$

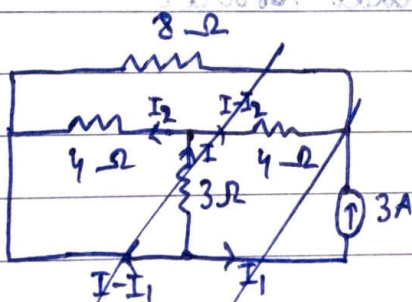

$$-3I - 4I_2 = 0$$


$$3I = -4I_2$$

$$-4I_2 + 8(I - I_2) + 4(I - I_2) = 0$$

$$I_2 = 3(I - I_2)$$

$$4I_2 = 3I$$



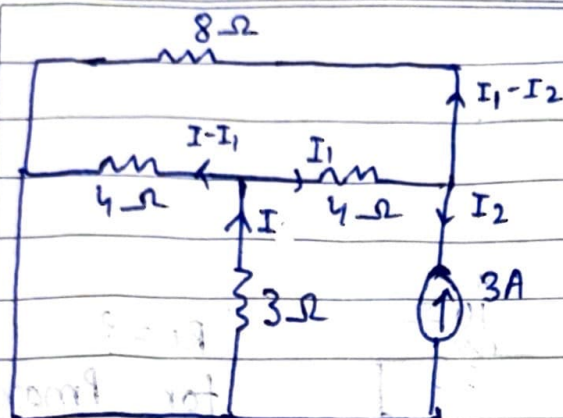

$$\begin{aligned}
 I_2 &= -3A \\
 -4I_1 - 8(I_1 - I_2) + 4(I - I_1) &= 0 \\
 -16I_1 + 8I_2 + 4I &= 0 \\
 I + 2I_2 &= 4I_1 \\
 I - 6 &= 4I_1 \\
 I - 4I_1 &= 6 \quad \text{--- (1)} \\
 -6I &= 6 \\
 I &= -1A
 \end{aligned}$$


$$\begin{aligned}
 3I + 4(I - I_1) &= 0 \\
 7I &= 4I_1
 \end{aligned}$$

By SPT  $I = 1 - 1 - 2 = -2A$

### → Maximum Power Transfer Theorem

The condition for maximum power to flow via load resistor  $R_L$  can be achieved when the  $R_L =$  Thevenin equivalent resistance of the ckt.

#### • derivation

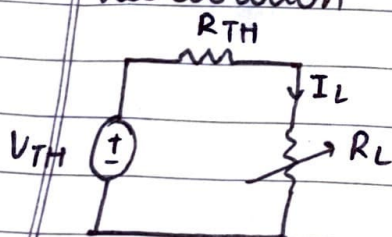

Power via  $R_L$

$$P = I_L^2 R_L$$

By Thevenin's theorem

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$P = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

diff wrt  $R_L$  &  $= 0$  for  $P_{max}$

$$\frac{dP}{dR_L} = V_{TH}^2 \left[ \frac{(R_{TH} + R_L)^2 - 2R_L(R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right] = 0$$

$$R_{TH} + R_L - 2R_L = 0$$

$R_{TH} = R_L$  → This is req condition



$$\Rightarrow \text{Power} = I_L^2 R_{TH}$$

$$A_2 = \frac{V_{TH}^2}{R_{TH}}$$

$$A_1 = \frac{V_{TH}^2}{4R_{TH}}$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$

$$I_{TH} = \frac{V_{TH}}{4R_{TH}}$$

$$I_{TH} = \frac{V_{TH}}{4R_{TH}}$$



$$10\Omega$$

$$R_L = ?$$

for  $P_{max}$

$$P_{max} = ?$$

Q

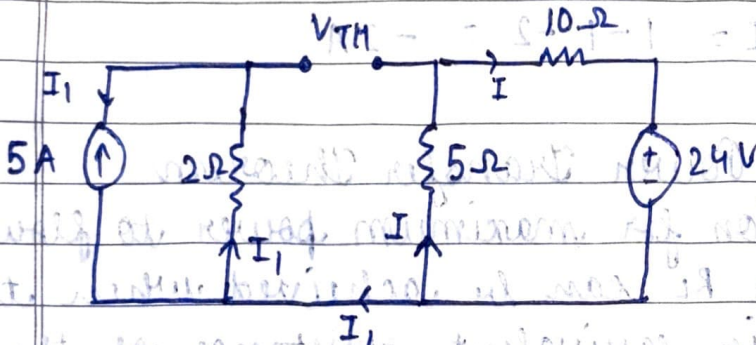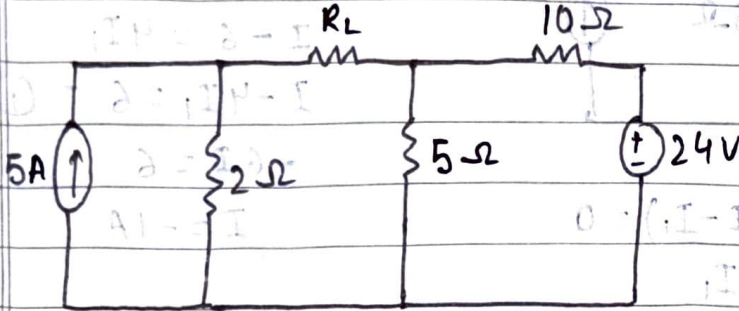


$$I_1 = +5A$$

$$-5I - 10I - 24 = 0$$

$$15I + 24 = 0$$


$$I = -8/5 = -1.6A$$

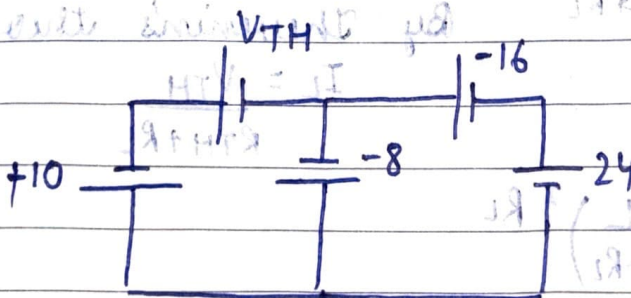

$$V_{TH} = (2V) \cdot 9\Omega - 5(9\Omega + 10\Omega) / (9\Omega + 10\Omega)$$

$$0 = 18\Omega - 9\Omega + 10\Omega$$



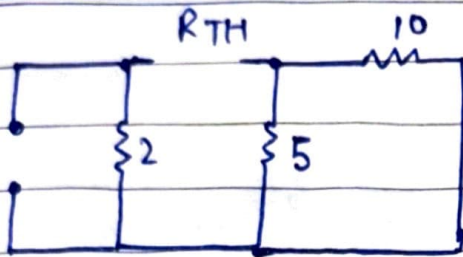



$$5 \parallel 10 + 2$$

$$\frac{10}{3} + 2 = \frac{16}{3} \Omega$$

$$R_{TH} = 5.33 \Omega$$

$$P_m = \frac{(2)^2 \times 3}{4 \times 16} = \frac{3}{16} \text{ W}$$

→ Star - Delta conversion

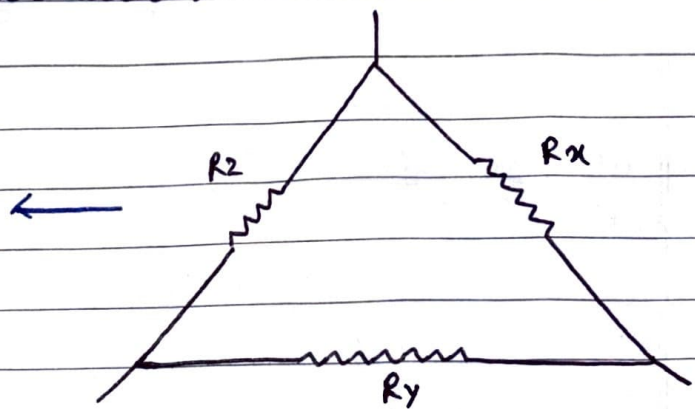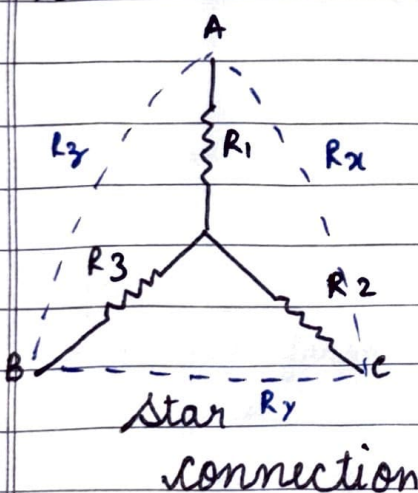

$$R_x = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_y = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_z = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$

For star to delta conversion